

Introduction:

A very simple and easy way to provide for human interaction with the microcontroller is to insert a button into the circuit. We communicate with computers using two main input devices: the mouse and the keyboard. A keyboard is nothing more than a bunch of buttons. Adding a button or switch to the circuit enables the microcontroller to receive human input.

In the first experiment, we've focused on output only. Now we're going to go to the other end of spectrum and play around with inputs. Push button switches are widely used in embedded system seen in very simple to highly complex systems. So, knowledge about interfacing them to any microcontroller is very essential in designing such systems. This lesson deals with the technicalities of push button interfacing with 8051 microcontroller and includes a simple example of microcontrollers digital Read function and then so as to ON and OFF an LED.

Hardware Discussion: Push Buttons

A **push-button** (also spelled pushbutton) or simply button or tactile switch is a component that connects two points

in a circuit when you press it. Buttons are typically made out of hard materials and its surface is usually flat or shaped to accommodate the human finger or hand, so as to be easily depressed or pushed.



Fig: Some of available Push Buttons

Push Button Features :

- Two state mechanism. Initially, it remains in off state or normally
- **open** state but when it is pressed, we can say it **close** state.
- Available Momentary and Latching types
- Available size, color, shape etc.
- Available in Vertical and Horizontal pin outs.
- High Durability
- Click response high.

A typical push button switch has two active terminals that may be normally open or closed and changes its state when pressed or depressed. Sometimes we get 4 pins with push buttons having a paired (internally connected)

terminals of each pin which is illustrated in the following figure. There are also some push buttons are normally closed but open when is pressed. Those are used for some special purposes.

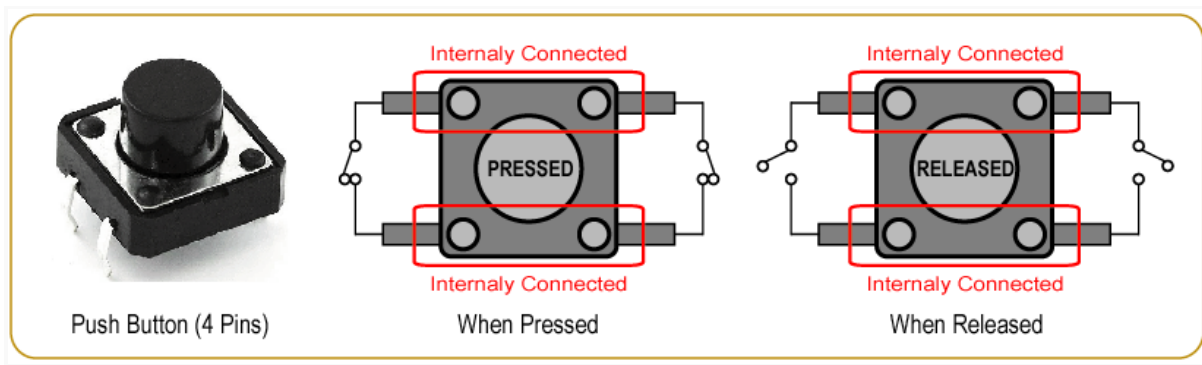


Fig: 4 Pin Push Button Connections and Actions

How it works?

If we connect the push button switch directly to a Microcontroller to get digital input, It means switch one pin is connected to Ground or 5v Vcc and another pin connected to 2 Microcontroller digital pin. In this case, the Microcontroller is read unstable input from the push button.

So, we need to connect a “pull-up” or “pull-down” resistors circuit to stabilizes the input, when using the switch.

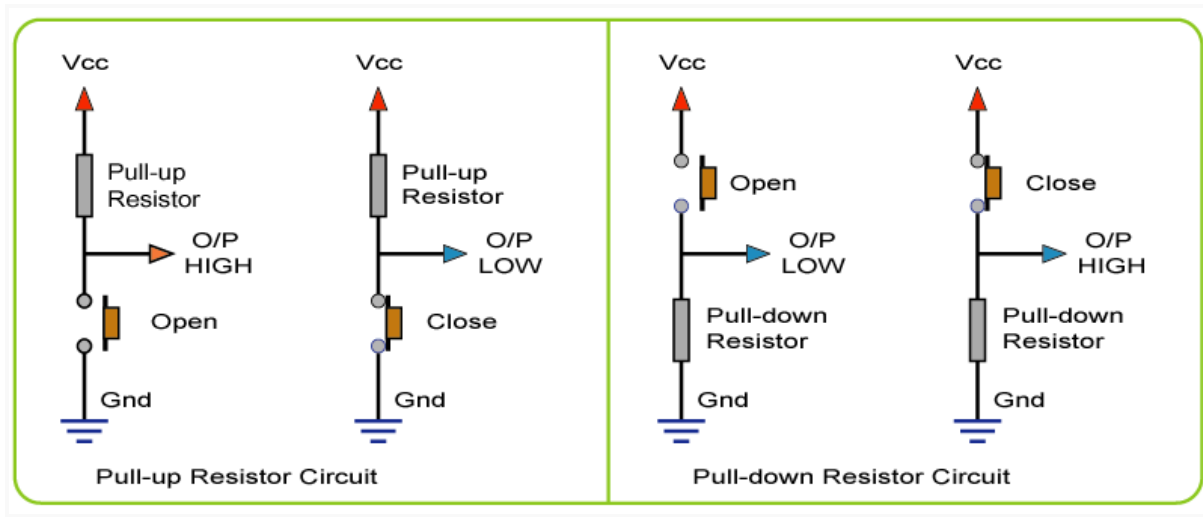


Fig: 4 Pin Push Button Connections and Actions

Pull-up Resistors : If the push button one pin is connected to the Vcc through a resistor and the other pin is connected to the ground, this circuit known as the pull-up resistor circuit. In this case, the push button output is High(1) when the button is open, and the output of the push button is Low(0) when the button is pressed.

Pull-down Resistors : If the push button one pin is connected to the ground through a resistor and the other pin is connected to the Vcc, this circuit known as the pull-down resistor circuit. In this case, the push button output is Low(0) when the button is open, and the output of the push button is High(1) when the button is pressed.

Circuit Diagram : Push Button Interfacing to 8051.

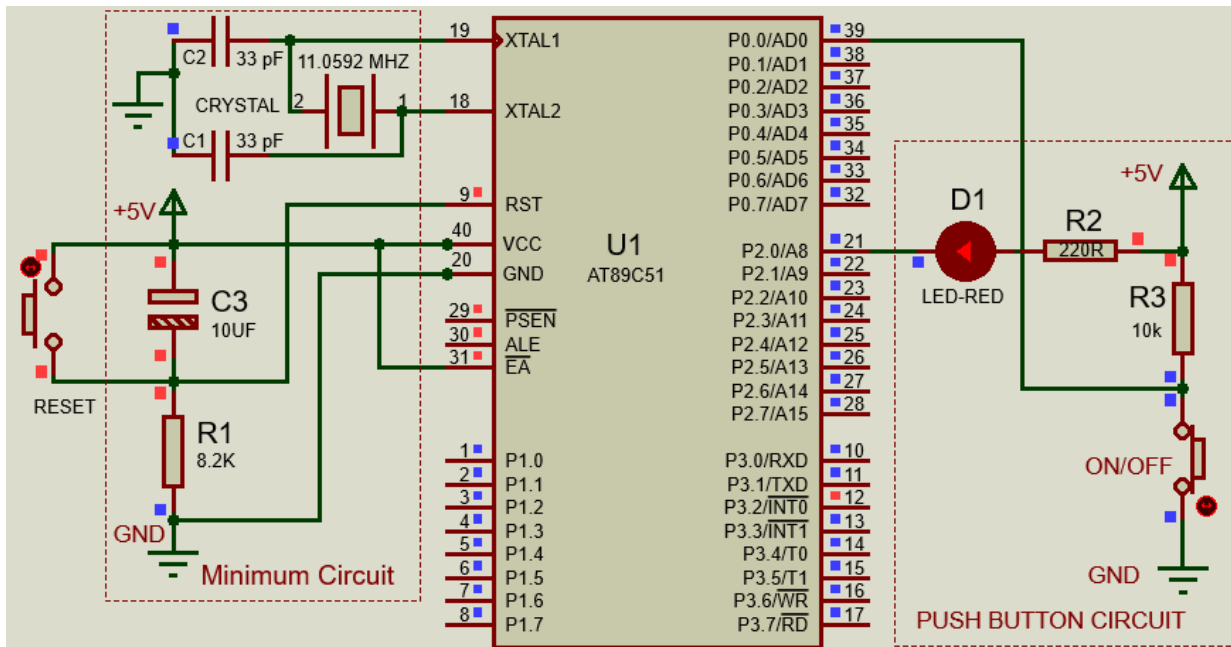


Fig: Push Button interfacing with AT89S51

Circuit Discussion :

A push button switch is connected to PORT-0 PIN-0. The SW is connected externally with a pull-up resistor since there is no internal pull-up resistor for port 0. The other end of the push button is connected to ground.

The voltages at the pins will be VCC (Approx) when the button is not pushed. The input pin will get grounded on pressing the button. The LED connected to the PORT-2 PIN-0 with a series resistor to limit the current. Our target is to ON the LED as long as the Button (ON) is pressed and hold and vice versa.

Assembly Program : Push Button Pull 8051.asm

```

LED    EQU    P2.0

        ORG    000H    ; starting address
        SJMP    MAIN    ; jumps to the LABEL
        ORG    003H    ; starting address for the ISR(INT0)
        ACALL    ISR    ; calls the ISR (interrupt service routine)
        RETI          ; returns from the interrupt

MAIN:    ; main function that sets the interrupt parameters
        MOV     P0,#00H
        MOV     P1,#00H
        MOV     P2,#00H
        MOV     P3,#00000100B

        MOV     IE,#081H    ; Enable INT0
        SETB    IT0    ; Set Falling Edge Trigger for INT0
        SJMP    $    ; jumps back to the MAIN subroutine

ISR:     ; interrupt service routine
        CPL     LED    ; complements the current value in accumulator A
        RET          ; jumps to RETI

        END
    
```

- **Home Task :** Design a circuit and write a program to perform as a 8 bit binary counter using 8 LEDS or 8 logic state terminal on any port. Additionally there should be three push buttons; for up count, downcount and reset operations.

